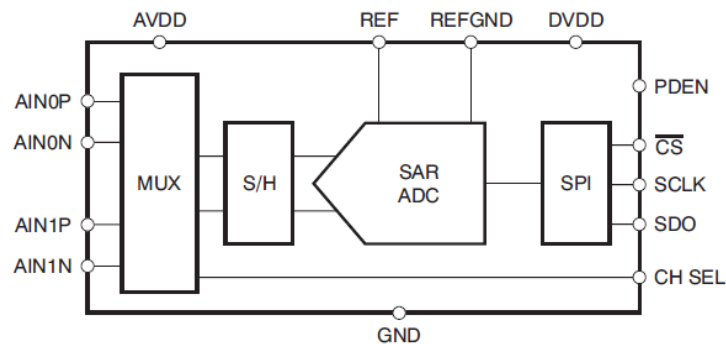


IE4-DS LAB SESSION #1: LECTURE PREPARATION


Surname, First Name	Group	Team
1. all of us	1 <input type="checkbox"/>	A B C D E F
2.	2 <input type="checkbox"/>	
3.	3 <input type="checkbox"/>	

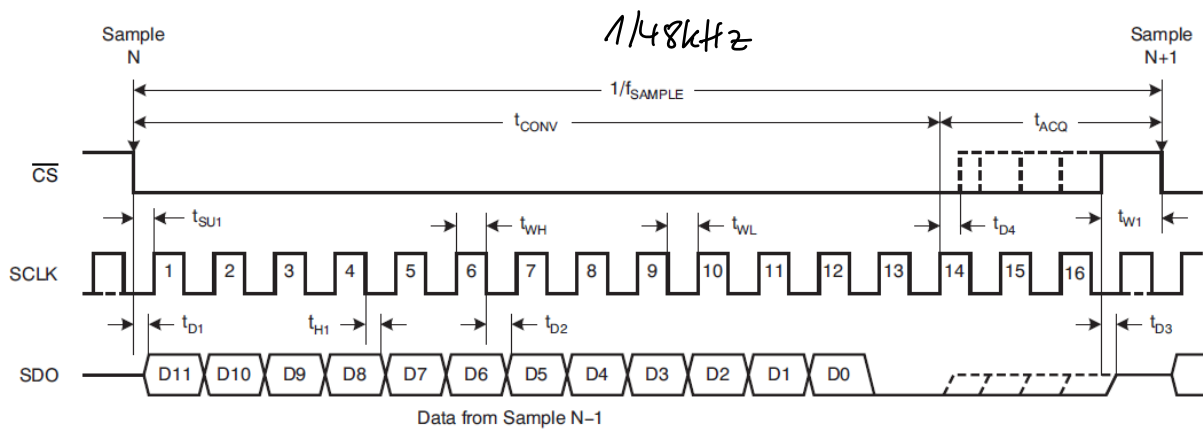TASK


Design a digital module ADCDAC_TOP in VHDL that reads data from an ADS7947 (<http://www.ti.com/lit/ds/symlink/ads7947.pdf>). The communication to the FPGA (Virtex 7 FPGA on an Xilinx ML507 board) is accomplished by a 3-wire synchronous serial transmission (SCLK, SDO, -CS).



The timing of the three signals is as follows (to read a 12-bit ADC value).



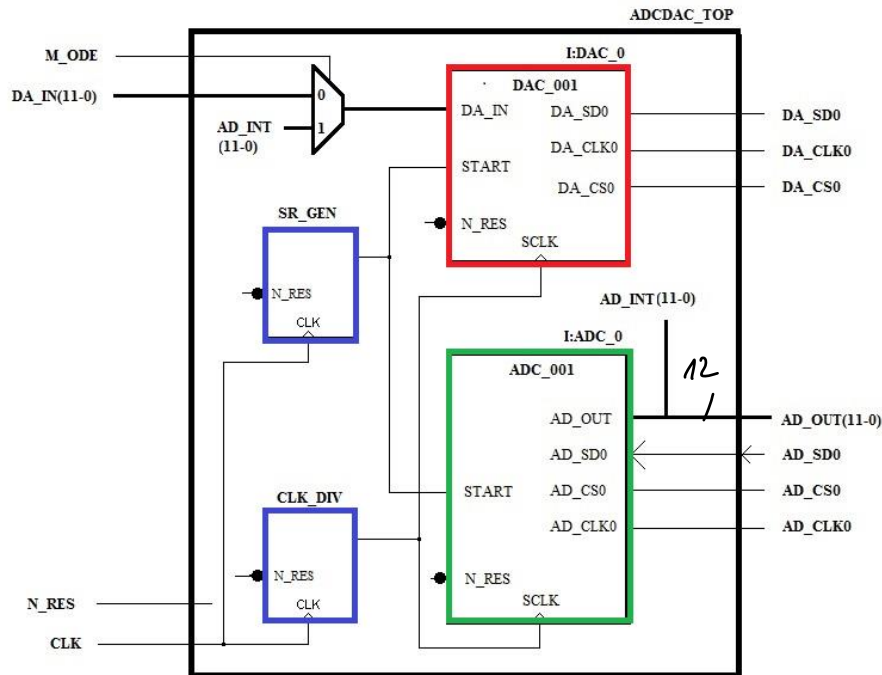The FPGA module ADCDAC_TOP shall have the following blocks:



The module ADC_001 that reads data from the ADC and converts them into a parallel 12bit word AD_OUT(11:0), a clock divider CLK_DIV for that generates a 3.125 MHz clock signal (which is clock speed of FPGA 100MHz / 32) and a sample rate generator module SR_GEN that generates every 1/48 kHz a START pulse that triggers a new reading of the external ADC. The DAC module will be done by yourself during prep of the lab.

TASK 1: DESIGN OF THE CLOCK DIVIDER CLK_DIV

Write a VHDL module CLK_DIV with a clock divider and simulate the module.

SPECIFICATION (VERBALLY)

- the clock divider shall generate SCLK with 3.125MHz generated from a global CLK with 100MHz
- a modulo-32 (5bit) counter shall be used of which the MSB is the SCLK output
- the module shall be reset by an active low asynchronous reset

SIMULATION TEST CASES (VERBALLY)

- verify for a least 3 periods that a 3.125 MHz output is generated
- verify that the reset is asynchronous by applying a reset not aligned to clock edges and that it is active low and that the CLK_CNT value is "00000" when reset
- verify that CLK_CNT increments correctly

VHDL MODEL

```
library IEEE;
use IEEE.std_logic_1164.ALL;
use IEEE.std_logic_unsigned.ALL;

entity CLK_DIV is
    port ( CLK, N_RES: in bit;      -- 100 MHz; async, active low reset
          SCLK      : out bit); -- 3.125 MHz clk out
end CLK_DIV;

architecture BEHAVIOUR of CLK_DIV is

    signal CLK_CNT : std_logic_vector(4 downto 0);
```

```

begin

-- clock divider
CLK_DIV : process(N_RES,CLK)
begin
    if N_RES ='0' then
        CLK_CNT <= (others =>'0');
    elsif CLK = '1' and CLK'event then
        CLK_CNT <= CLK_CNT + '1' ;
    end if;
end process CLK_DIV;

SCLK <= to_bit(CLK_CNT(4)) ;

end BEHAVIOUR ;

```

TEST BENCH

```

# show input signals
add wave -divider -height 32 Inputs
add wave -height 30 -radix default N_RES
add wave -height 30 -radix default CLK


# show internal signals
add wave -height 30 -radix default CLK_CNT

# show output signals
add wave -height 30 -radix default SCLK

# generate input stimuli
force CLK      0 0ns, 1 5ns -r 10ns
force N_RES    1 0ns, 0 33ns, 1 57ns
run 1000ns

```

SIMULATION RESULTS

 

TASK 2: DESIGN OF THE SAMPLING RATE GENRATOR SR_GEN

Write a VHDL module SR_GEN that generates the START_TE pulse at a rate of 48kHz and simulate the module.

SPECIFICATION (VERBALLY)

- sample rate generator shall generate a START pulse of 320ns duration (32/100MHz) at a frequency of 48 kHz
- a counter shall be used to generate period and duty cycle of START signal
- the module shall be reset by an active low asynchronous reset

SIMULATION TEST CASES (VERBALLY)

- verify for a least 3 periods that a pulse every $1/48\text{kHz} = 20.8333\ldots\mu\text{s}$ is generated
- verify that the reset is asynchronous by applying a reset not aligned to clock edges and that it is active low and that the CLK_CNT value is "00000" when reset
- verify that CLK_CNT increments correctly

VHDL MODEL

```
library IEEE;
use IEEE.std_logic_1164.ALL;
use IEEE.std_logic_unsigned.ALL;

entity SR_GEN is
    port ( CLK, N_RES : in bit; -- 100MHz; async, active low reset
          START_TE    : out bit);
end SR_GEN;

architecture BEHAVIOUR of SR_GEN is

    signal SCNT : std_logic_vector(11 downto 0);

begin

    SR_GEN:process(N_RES,CLK)
    begin
        if N_RES ='0' then
            SCNT <= (others=>'0');
        elsif CLK = '1' and CLK'event then
            if SCNT = "100000100010" then -- 100MHz/48kHz=2083.33
                                           -- range 0...2082
                SCNT <= (others=>'0');
            else
                SCNT <= SCNT + '1' ;
            end if;
        end if;
    end process SR_GEN;
    START_TE <= '1' when SCNT < "000000100000" else '0' after 5 ns;

end BEHAVIOUR ;
```

TEST BENCH


```
# show input signals
add wave -divider -height 32 Inputs
add wave -height 30 -radix default N_RES
add wave -height 30 -radix default CLK

# show internal signals
add wave -divider -height 32 Internals
add wave -height 30 -radix default SCNT

# show output signals
add wave -divider -height 32 Outputs
add wave -height 30 -radix default START_TE

# generate input stimuli
force CLK      0 0ns, 1 5ns -r 10ns
force N_RES    1 0ns, 0 33ns, 1 57ns
run 70000ns
```

SIMULATION RESULTS

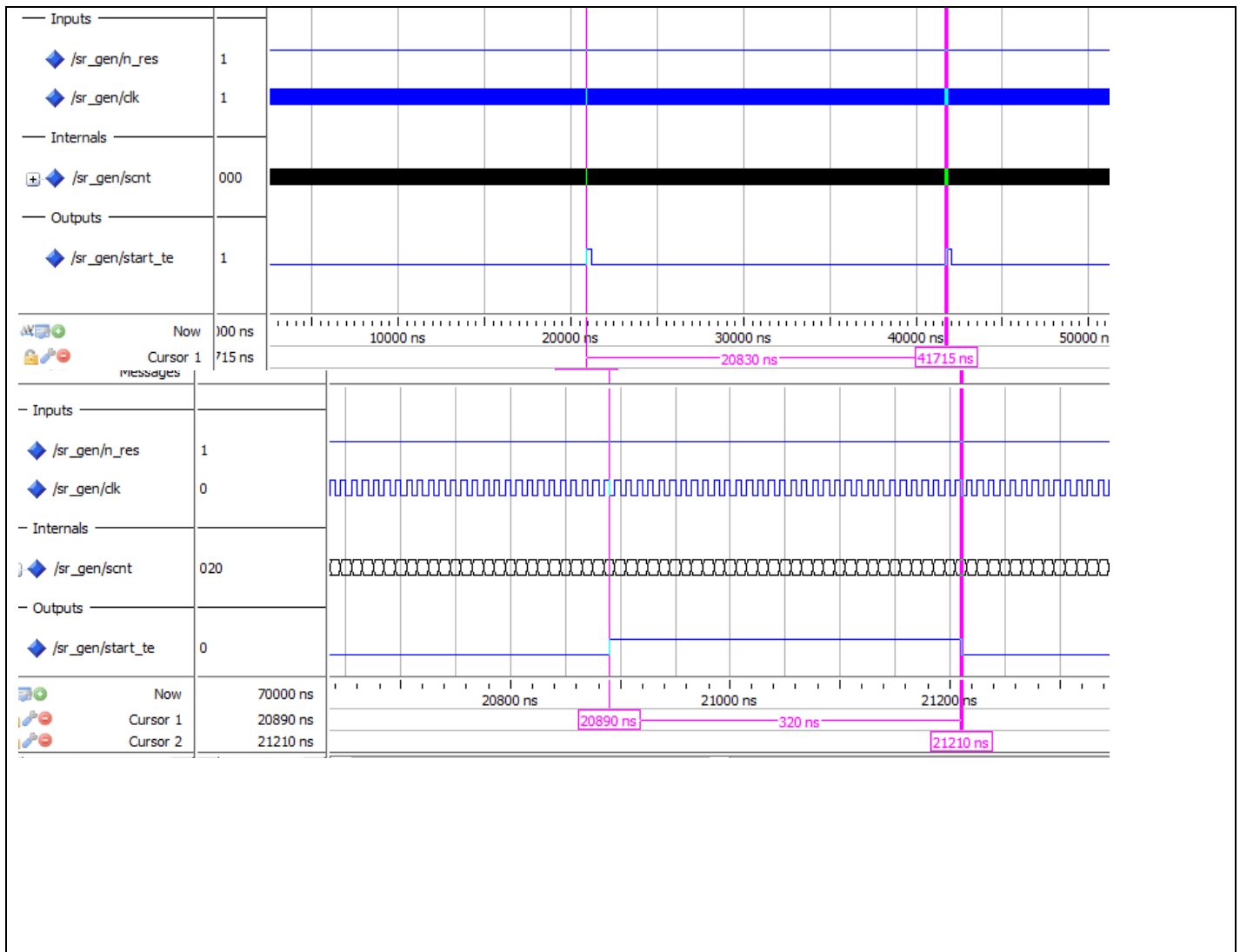


TASK 3: DESIGN OF THE ADC COMMUNICATION MODULE


Write a VHDL module ADC_001 that controls AD_CLK0 and AD_CS0 of the ADC and receives data AD_SD0. The module shall convert the serial bit stream from the ADC into a parallel 12bit data word.

SPECIFICATION (VERBALLY)

 - The serial bit stream is initiated and read by an FSM and a counter BIT_CNT
- When the FSM is in AD_IDLE it waits for a next sampling point (START='1')
- After START='1', -CS is pulled low and 16 bits are read (12 data bits plus 4 zeros for acquisition phase) in state Shift_AD



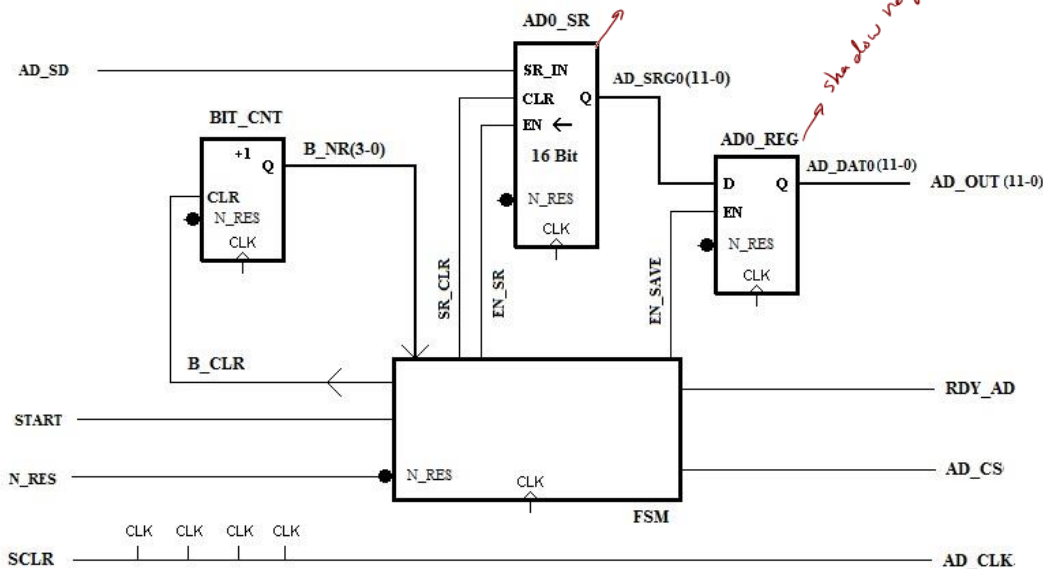- Received values are shifted into shift register AD0_SR (MSB first)



- -CS is pulled high afterwards and contents of shift register is copied to AD0_REG (highest 12 bits) in state SAVE_AD
- SR_CLR clears the shift register
- Shifting is done when EN_SR=1

SIMULATION TEST CASES (VERBALLY)

- After reset the FSM is in IDLE_AD
- With START=1 the FSM transits from IDLE_AD to SHIFT_AD
- In state SHIFT_ADD 16 values are read in correctly from ADC (input voltage needs to be known), 4 zeros correctly appended
- After reading 16 values, the FSM transits to SAVE_AD
- In SAVE_AD the 12bit value is shifted to AD0_REG
- BIT_CNT is correctly cleared when ADC value was read in
- Next 16bit ADC sample is correctly read in after sample period 1/48kHz

VHDL MODEL

```

library IEEE;
use IEEE.std_logic_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity ADC_001 is
    port ( SCLK, N_RES : in bit;
          AD_OUT      : out bit_vector(11 downto 0);
          START       : in bit; -- start signal
          RDY_AD      : out bit ; -- ready flag
          AD_SD       : in bit ;
          AD_CS       : out bit ;
          AD_CLK      : out bit );
end ADC_001 ;

architecture BEHAVIOUR of ADC_001 is
    -- bit counter
    signal B_NR      : unsigned(3 downto 0):= "0000" ;
    signal B_CLR     : bit ;

    --Control Signals ADC
    signal SR_CLR    : bit; -- clear shift reg
    signal EN_SR     : bit; -- enable shift reg
    signal EN_SAVE   : bit; -- store

    -- registers for ADC data
    signal AD_SRG0   : bit_vector(15 downto 0):= (others => '0') ; -- shift reg
    signal AD_DAT0   : bit_vector(11 downto 0):= (others => '0') ; -- save reg

    type State_Type_AD is (IDLE_AD,SHIFT_AD,SAVE_AD);
    -- states of ADC communication module
    signal AD_STATE   : State_Type_AD;

```

```

signal  AD_NEXTSTATE      : State_Type_AD;

begin

AD_OUT <= AD_DAT0;

-- clock to ADC
AD_CLK <= not SCLK;

-- counter for serial bits -----
BIT_CNT: process(SCLK)
begin
    if SCLK = '1' and SCLK'event then
        if B_CLR = '1' then
            B_NR <= "0000" after 5 ns ;
        else
            B_NR <= B_NR + 1 after 5 ns ;
        end if ;
    end if ;
end process BIT_CNT;

-----ADC0 - shift / save regs -----
AD0_SR: process(SCLK, N_RES)
begin
    if N_RES = '0' then
        AD_SRG0 <= (others=>'0') after 5 ns ;
    elsif SCLK = '1' and SCLK'event then
        if SR_CLR = '1' then
            AD_SRG0 <= (others=>'0') after 5 ns ;
        elsif EN_SR = '1' then
            AD_SRG0 <= AD_SRG0(14 downto 0) & AD_SD after 5 ns ;
        end if;
    end if ;
end process AD0_SR;

AD0_REG: process(SCLK, N_RES)
begin
    if N_RES = '0' then
        AD_DAT0 <= (others=>'0') after 5 ns ;
    elsif SCLK = '1' and SCLK'event then
        if EN_SAVE = '1' then
            AD_DAT0 <= AD_SRG0(15 downto 4) after 5 ns ;
        end if;
    end if ;
end process AD0_REG;

-- FSM_ADC comm module -----
FSM_AD_REG : process(SCLK , N_RES)
begin
    if N_RES = '0' then
        AD_STATE <= IDLE_AD after 5 ns ;
    elsif SCLK = '1' and SCLK'event then
        AD_STATE <= AD_NEXTSTATE after 5 ns ;
    end if ;
end process ;

FSM_AD_SN : process(AD_STATE,B_NR,START)
begin
    AD_NEXTSTATE <= AD_STATE after 5 ns ;
    AD_CS <= '1' after 5 ns ;
    EN_SR <= '0' after 5 ns ;
    SR_CLR <= '0' after 5 ns ;
    EN_SAVE <= '0' after 5 ns ;
    RDY_AD <= '0' after 5 ns ;
    B_CLR <= '1' after 5 ns ;
    case AD_STATE is
        when IDLE_AD => SR_CLR <= '1' after 5 ns ;
                                RDY_AD <= '1' after 5 ns ;
                                if START = '1' then
                                    AD_NEXTSTATE <= SHIFT_AD after 5 ns ;
                                end if ;
        when SHIFT_AD => AD_CS <= '0' after 5 ns ; -- 15 states

```

```

        EN_SR <= '1' after 5 ns ;
        B_CLR <= '0' after 5 ns ;
    if B_NR = "1111" then
        B_CLR <= '1' after 5 ns ;
        AD_NEXTSTATE <= SAVE_AD after 5 ns ;
    end if;
    when SAVE_AD => EN_SAVE <= '1' after 5 ns ;
        if START = '0' then
            AD_NEXTSTATE <= IDLE_AD after 5 ns ;
        end if;
    end case;
end process;

end BEHAVIOUR ;

```

TEST BENCH

Does not cover all relevant cases (!)

```

# --- compilation
vlib work
vcom -93 -work work ADC_001.vhd
vsim ADC_001
# --- simulation
# view signal wave forms
view wave
# number format is hex
radix hex

# show input signals
add wave -divider -height 32 Inputs
add wave -height 30 -radix default N_RES
add wave -height 30 -radix default SCLK
add wave -height 30 -radix default START

# show reg signals
add wave -divider -height 32 Reg
add wave -height 30 -radix default AD_SRQ0
add wave -height 30 -radix default AD_DAT0

# show ADC signals
add wave -divider -height 32 ADC_signals
add wave -height 30 -radix default AD_CS
add wave -height 30 -radix default AD_CLK
add wave -height 30 -radix default AD_SD

# show output of register
add wave -divider -height 32 Reg_output
add wave -height 30 -radix default AD_OUT

# generate input stimuli
force SCLK    0 0ns, 1 160ns -r 320ns
force N_RES   1 0ns, 0 33ns, 1 57ns
force START   0 0ns, 1 1000ns, 0 1320ns
force AD_SD   0 0ns, 1 1320ns, 0 1640ns, 1 1960ns, 0 2600ns, 1 2920ns, 0 3240ns
run 8000ns

```

SIMULATION RESULTS

